Complete the maze by connecting the LED to the battery and closing the circuit!

start

finish